

## ENGINEERING ELECTROMAGNETICS


HW 3: Due Friday, 27 January

2.11, 2.13, 2.14, 2.17, 2.19, 2.27, 2.31, 2.33, 2.34, 2.40, 2.44, 2.47, 2.53

**Problem 2.11** A  $50\text{-}\Omega$  microstrip line uses a  $0.6\text{-mm}$  alumina substrate with  $\epsilon_r = 9$ . Use CD Module 2.3 to determine the required strip width  $w$ . Include a printout of the screen display.

**Solution:** According to the solution provided by CD Module 2.3, the required strip width is

$$w = 0.613 \text{ mm.}$$

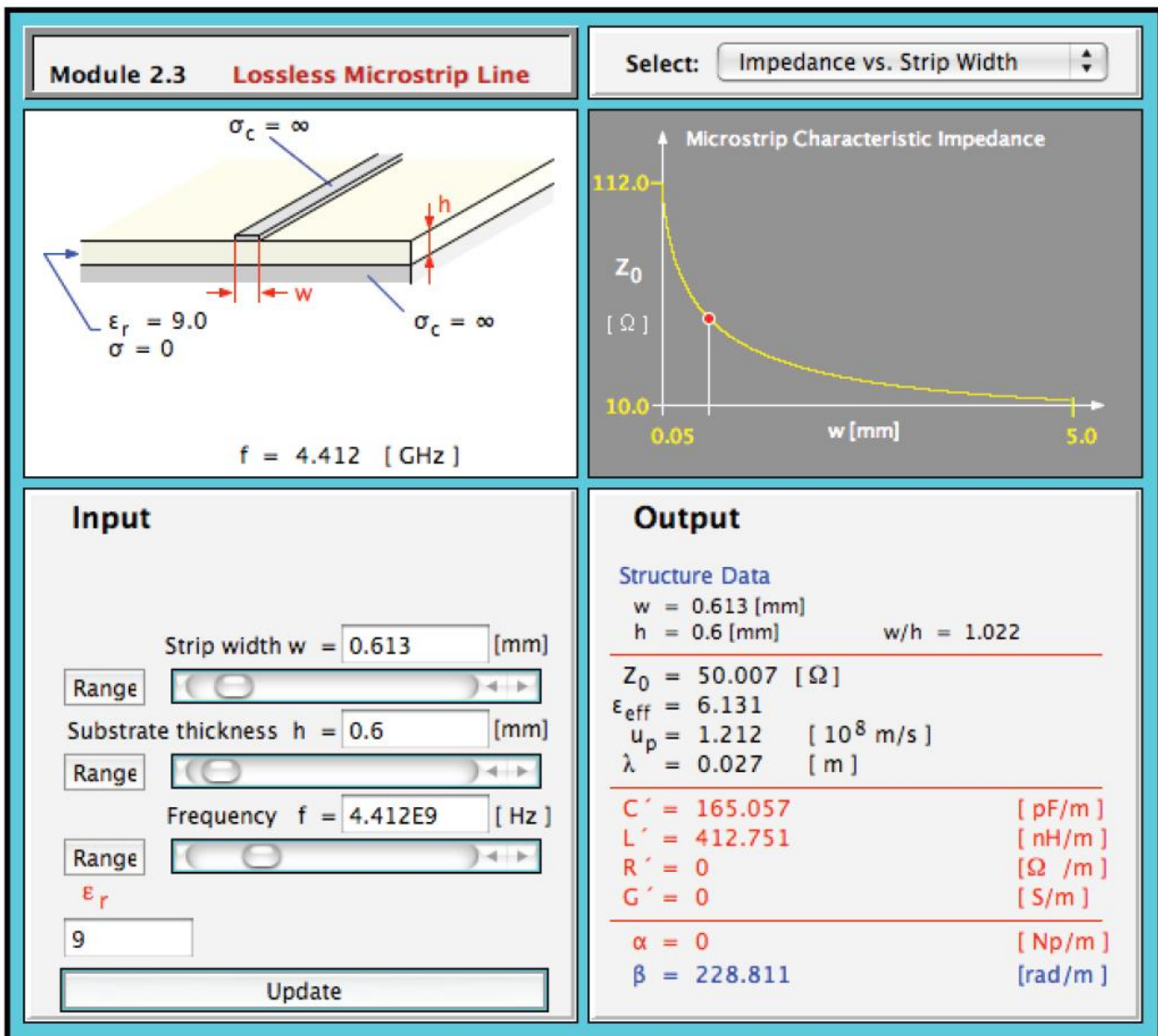

**Problem 2.13** In addition to not dissipating power, a lossless line has two important features: (1) it is dispersionless ( $\mu_p$  is independent of frequency) and (2) its characteristic impedance  $Z_0$  is purely real. Sometimes, it is not possible to design a transmission line such that  $R' \ll \omega L'$  and  $G' \ll \omega C'$ , but it is possible to choose the dimensions of the line and its material properties so as to satisfy the condition

$$R'C' = L'G' \quad (\text{distortionless line}).$$

Such a line is called a *distortionless* line because despite the fact that it is not lossless, it does nonetheless possess the previously mentioned features of the loss line. Show that for a distortionless line,

$$\alpha = R' \sqrt{\frac{C'}{L'}} = \sqrt{R'G'}, \quad \beta = \omega \sqrt{L'C'}, \quad Z_0 = \sqrt{\frac{L'}{C'}}.$$

**Solution:** Using the distortionless condition in Eq. (2.22) gives

$$\begin{aligned} \gamma &= \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{G'}{C'} + j\omega\right)} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{R'}{L'} + j\omega\right)} \\ &= \sqrt{L'C'} \left(\frac{R'}{L'} + j\omega\right) = R' \sqrt{\frac{C'}{L'}} + j\omega \sqrt{L'C'}. \end{aligned}$$

Hence,

$$\alpha = \Re(\gamma) = R' \sqrt{\frac{C'}{L'}}, \quad \beta = \Im(\gamma) = \omega \sqrt{L'C'}, \quad u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}.$$

Similarly, using the distortionless condition in Eq. (2.29) gives

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{L'}{C'}} \sqrt{\frac{R'/L' + j\omega}{G'/C' + j\omega}} = \sqrt{\frac{L'}{C'}}.$$


---

**Problem 2.14** For a distortionless line [see Problem 2.13] with  $Z_0 = 50 \Omega$ ,  $\alpha = 20$  (mNp/m),  $u_p = 2.5 \times 10^8$  (m/s), find the line parameters and  $\lambda$  at 100 MHz.

**Solution:** The product of the expressions for  $\alpha$  and  $Z_0$  given in Problem 2.6 gives

$$R' = \alpha Z_0 = 20 \times 10^{-3} \times 50 = 1 \quad (\Omega/\text{m}),$$

and taking the ratio of the expression for  $Z_0$  to that for  $u_p = \omega/\beta = 1/\sqrt{L'C'}$  gives

$$L' = \frac{Z_0}{u_p} = \frac{50}{2.5 \times 10^8} = 2 \times 10^{-7} \text{ (H/m)} = 200 \quad (\text{nH/m}).$$

With  $L'$  known, we use the expression for  $Z_0$  to find  $C'$ :

$$C' = \frac{L'}{Z_0^2} = \frac{2 \times 10^{-7}}{(50)^2} = 8 \times 10^{-11} \text{ (F/m)} = 80 \quad (\text{pF/m}).$$

The distortionless condition given in Problem 2.6 is then used to find  $G'$ .

$$G' = \frac{R'C'}{L'} = \frac{1 \times 80 \times 10^{-12}}{2 \times 10^{-7}} = 4 \times 10^{-4} \text{ (S/m)} = 400 \quad (\mu\text{S/m}),$$

and the wavelength is obtained by applying the relation

$$\lambda = \frac{u_p}{f} = \frac{2.5 \times 10^8}{100 \times 10^6} = 2.5 \text{ m}.$$

**Problem 2.17** Using a slotted line, the voltage on a lossless transmission line was found to have a maximum magnitude of 1.5 V and a minimum magnitude of 0.6 V. Find the magnitude of the load's reflection coefficient.

**Solution:** From the definition of the Standing Wave Ratio given by Eq. (2.73),

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1.5}{0.6} = 2.5.$$

Solving for the magnitude of the reflection coefficient in terms of  $S$ , as in Example 2-5,

$$|\Gamma| = \frac{S-1}{S+1} = \frac{2.5-1}{2.5+1} = 0.43.$$

**Problem 2.19** A  $50\text{-}\Omega$  lossless transmission line is terminated in a load with impedance  $Z_L = (30 - j50)\text{ }\Omega$ . The wavelength is 8 cm. Find:

- (a) the reflection coefficient at the load,
- (b) the standing-wave ratio on the line,
- (c) the position of the voltage maximum nearest the load,
- (d) the position of the current maximum nearest the load.
- (e) Verify quantities in parts (a)–(d) using CD Module 2.4. Include a printout of the screen display.

**Solution:**

- (a) From Eq. (2.59),

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(30 - j50) - 50}{(30 - j50) + 50} = 0.57e^{-j79.8^\circ}.$$

- (b) From Eq. (2.73),

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.57}{1 - 0.57} = 3.65.$$

- (c) From Eq. (2.70)

$$\begin{aligned} d_{\max} &= \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2} = \frac{-79.8^\circ \times 8\text{ cm}}{4\pi} \frac{\pi\text{ rad}}{180^\circ} + \frac{n \times 8\text{ cm}}{2} \\ &= -0.89\text{ cm} + 4.0\text{ cm} = 3.11\text{ cm}. \end{aligned}$$

- (d) A current maximum occurs at a voltage minimum, and from Eq. (2.72),

$$d_{\min} = d_{\max} - \lambda/4 = 3.11\text{ cm} - 8\text{ cm}/4 = 1.11\text{ cm}.$$

(e) The problem statement does not specify the frequency, so in Module 2.4 we need to select the combination of  $f$  and  $\epsilon_r$  such that  $\lambda = 5\text{ cm}$ . With  $\epsilon_r$  chosen as 1,

$$f = \frac{c}{\lambda} = \frac{3 \times 10^8}{8 \times 10^{-2}} = 3.75\text{ GHz}.$$

The generator parameters are irrelevant to the problem.

The results listed in the output screens are very close to those given in parts (a) through (d).

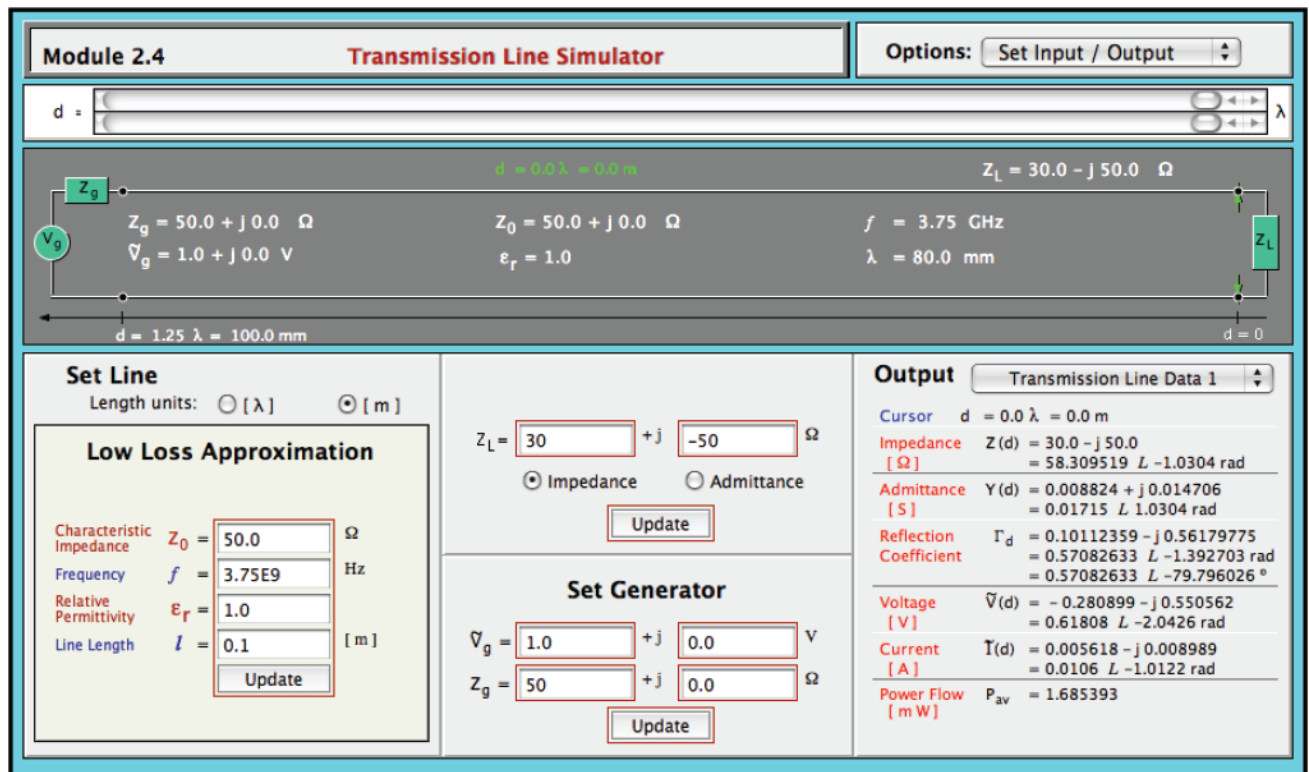


Figure P2.19(a)

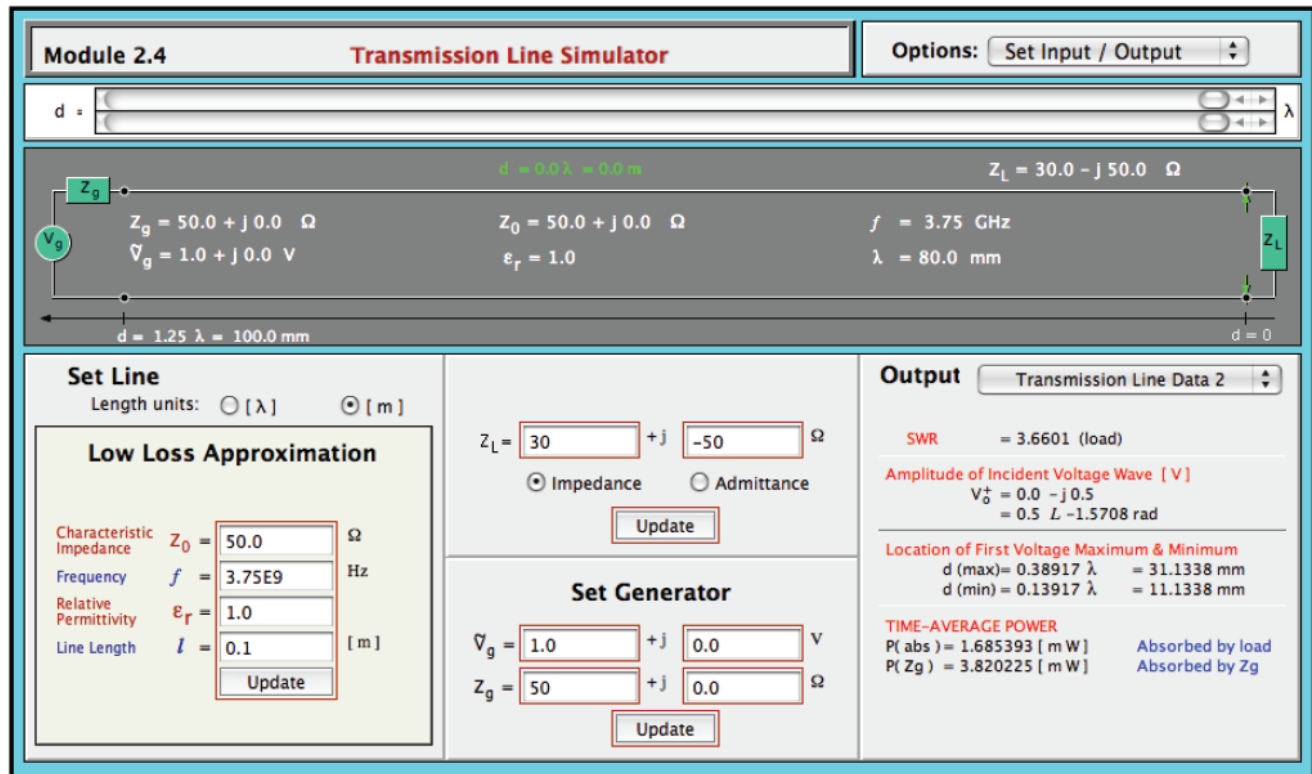


Figure P2.19(b)

**Problem 2.27** At an operating frequency of 300 MHz, a lossless 50- $\Omega$  air-spaced transmission line 2.5 m in length is terminated with an impedance  $Z_L = (40 + j20) \Omega$ . Find the input impedance.

**Solution:** Given a lossless transmission line,  $Z_0 = 50 \Omega$ ,  $f = 300 \text{ MHz}$ ,  $l = 2.5 \text{ m}$ , and  $Z_L = (40 + j20) \Omega$ . Since the line is air filled,  $u_p = c$  and therefore, from Eq. (2.48),

$$\beta = \frac{\omega}{u_p} = \frac{2\pi \times 300 \times 10^6}{3 \times 10^8} = 2\pi \text{ rad/m}.$$

Since the line is lossless, Eq. (2.79) is valid:

$$\begin{aligned} Z_{\text{in}} &= Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) = 50 \left[ \frac{(40 + j20) + j50 \tan(2\pi \text{ rad/m} \times 2.5 \text{ m})}{50 + j(40 + j20) \tan(2\pi \text{ rad/m} \times 2.5 \text{ m})} \right] \\ &= 50 [(40 + j20) + j50 \times 0] / [50 + j(40 + j20) \times 0] \\ &= (40 + j20) \Omega. \end{aligned}$$

**Problem 2.31** A voltage generator with

$$v_g(t) = 5 \cos(2\pi \times 10^9 t) \text{ V}$$

and internal impedance  $Z_g = 50 \Omega$  is connected to a 50- $\Omega$  lossless air-spaced transmission line. The line length is 5 cm and the line is terminated in a load with impedance  $Z_L = (100 - j100) \Omega$ . Determine:

- (a)  $\Gamma$  at the load.
- (b)  $Z_{\text{in}}$  at the input to the transmission line.
- (c) The input voltage  $\tilde{V}_i$  and input current  $\tilde{I}_i$ .
- (d) The quantities in (a)–(c) using CD Modules 2.4 or 2.5.



**Solution:**

(a) From Eq. (2.59),

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 - j100) - 50}{(100 - j100) + 50} = 0.62e^{-j29.7^\circ}.$$

(b) All formulae for  $Z_{in}$  require knowledge of  $\beta = \omega/u_p$ . Since the line is an air line,  $u_p = c$ , and from the expression for  $v_g(t)$  we conclude  $\omega = 2\pi \times 10^9$  rad/s. Therefore

$$\beta = \frac{2\pi \times 10^9 \text{ rad/s}}{3 \times 10^8 \text{ m/s}} = \frac{20\pi}{3} \text{ rad/m}.$$

Then, using Eq. (2.79),


$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) \\ &= 50 \left[ \frac{(100 - j100) + j50 \tan \left( \frac{20\pi}{3} \text{ rad/m} \times 5 \text{ cm} \right)}{50 + j(100 - j100) \tan \left( \frac{20\pi}{3} \text{ rad/m} \times 5 \text{ cm} \right)} \right] \\ &= 50 \left[ \frac{(100 - j100) + j50 \tan \left( \frac{\pi}{3} \text{ rad} \right)}{50 + j(100 - j100) \tan \left( \frac{\pi}{3} \text{ rad} \right)} \right] = (12.5 - j12.7) \Omega. \end{aligned}$$

(c) In phasor domain,  $\tilde{V}_g = 5 \text{ V}e^{j0^\circ}$ . From Eq. (2.80),


$$\tilde{V}_i = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = \frac{5 \times (12.5 - j12.7)}{50 + (12.5 - j12.7)} = 1.40e^{-j34.0^\circ} \text{ (V)},$$

and also from Eq. (2.80),
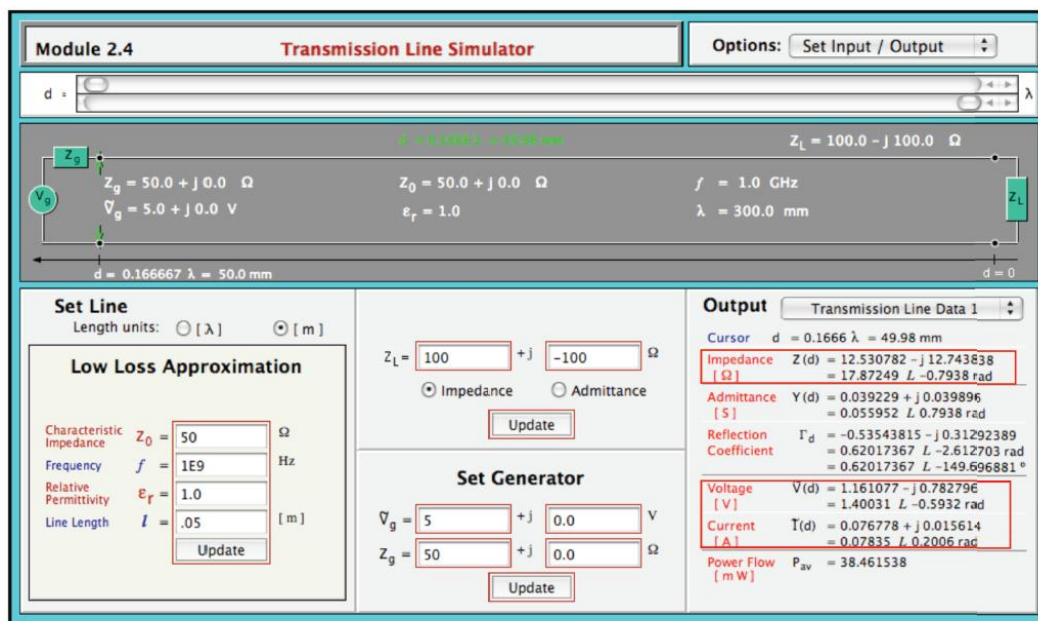
$$\tilde{I}_i = \frac{\tilde{V}_i}{Z_{in}} = \frac{1.4e^{-j34.0^\circ}}{(12.5 - j12.7)} = 78.4e^{j11.5^\circ} \text{ (mA)}.$$



**Problem 2.33** Two half-wave dipole antennas, each with an impedance of  $75\ \Omega$ , are connected in parallel through a pair of transmission lines, and the combination is connected to a feed transmission line, as shown in Fig. P2.33.

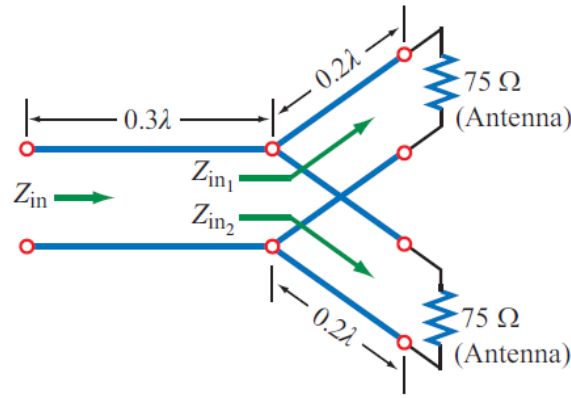

**Figure P2.33:** Circuit for Problem 2.33.

All lines are  $50\ \Omega$  and lossless.

- Calculate  $Z_{in1}$ , the input impedance of the antenna-terminated line, at the parallel juncture.
- Combine  $Z_{in1}$  and  $Z_{in2}$  in parallel to obtain  $Z'_L$ , the effective load impedance of the feedline.
- Calculate  $Z_{in}$  of the feedline.

**Solution:**


(a)

$$\begin{aligned} Z_{in1} &= Z_0 \left[ \frac{Z_{L1} + jZ_0 \tan \beta l_1}{Z_0 + jZ_{L1} \tan \beta l_1} \right] \\ &= 50 \left\{ \frac{75 + j50 \tan[(2\pi/\lambda)(0.2\lambda)]}{50 + j75 \tan[(2\pi/\lambda)(0.2\lambda)]} \right\} = (35.20 - j8.62)\ \Omega. \end{aligned}$$

(b)

$$Z'_L = \frac{Z_{in1} Z_{in2}}{Z_{in1} + Z_{in2}} = \frac{(35.20 - j8.62)^2}{2(35.20 - j8.62)} = (17.60 - j4.31)\ \Omega.$$

(c)

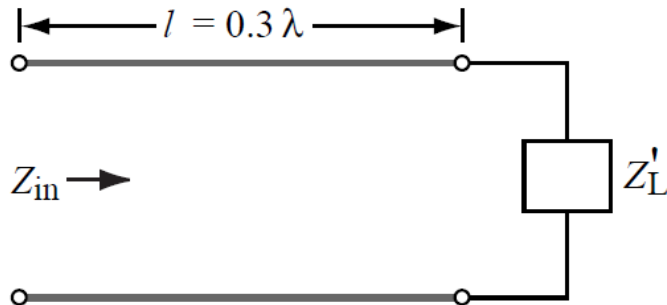


**Figure P2.33:** (b) Equivalent circuit.

$$Z_{in} = 50 \left\{ \frac{(17.60 - j4.31) + j50 \tan[(2\pi/\lambda)(0.3\lambda)]}{50 + j(17.60 - j4.31) \tan[(2\pi/\lambda)(0.3\lambda)]} \right\} = (107.57 - j56.7)\ \Omega.$$



**Problem 2.34** A  $50\text{-}\Omega$  lossless line is terminated in a load impedance  $Z_L = (30 - j20)\text{ }\Omega$ .

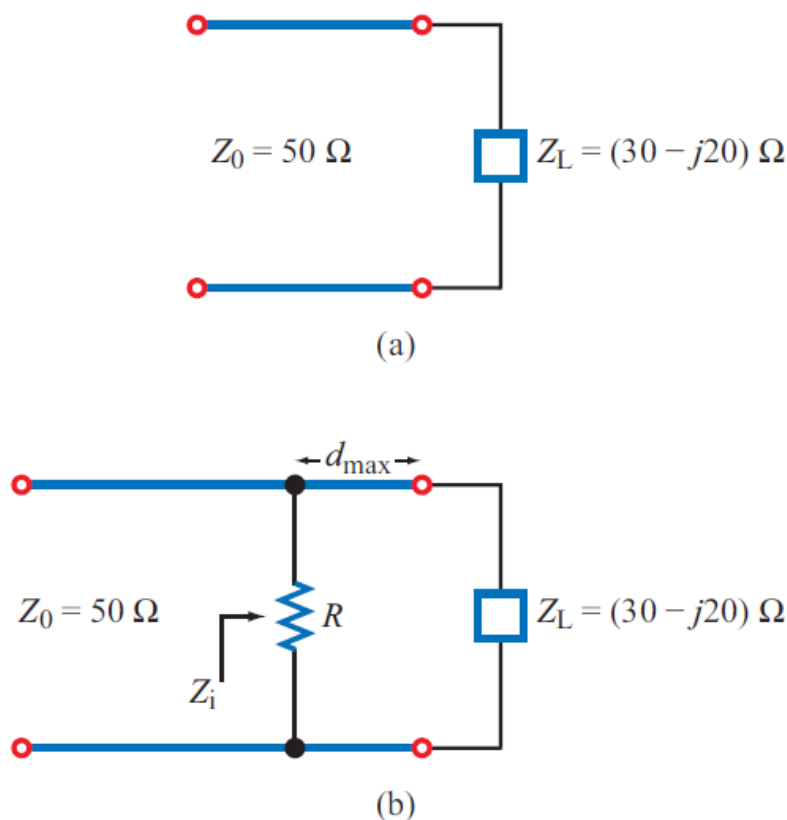

**Figure P2.34:** Circuit for Problem 2.34.

- (a) Calculate  $\Gamma$  and  $S$ .
- (b) It has been proposed that by placing an appropriately selected resistor across the line at a distance  $d_{\max}$  from the load (as shown in Fig. P2.34(b)), where  $d_{\max}$  is the distance from the load of a voltage maximum, then it is possible to render  $Z_i = Z_0$ , thereby eliminating reflection back to the end. Show that the proposed approach is valid and find the value of the shunt resistance.

**Solution:**

(a)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - j20 - 50}{30 - j20 + 50} = \frac{-20 - j20}{80 - j20} = \frac{-(20 + j20)}{80 - j20} = 0.34e^{-j121^\circ}.$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.34}{1 - 0.34} = 2.$$

(b) We start by finding  $d_{\max}$ , the distance of the voltage maximum nearest to the load. Using (2.70) with  $n = 1$ ,

$$d_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2} = \left( \frac{-121^\circ \pi}{180^\circ} \right) \frac{\lambda}{4\pi} + \frac{\lambda}{2} = 0.33\lambda.$$

Applying (2.79) at  $d = d_{\max} = 0.33\lambda$ , for which  $\beta l = (2\pi/\lambda) \times 0.33\lambda = 2.07$  radians, the value of  $Z_{\text{in}}$  before adding the shunt resistance is:

$$\begin{aligned} Z_{\text{in}} &= Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) \\ &= 50 \left( \frac{(30 - j20) + j50 \tan 2.07}{50 + j(30 - j20) \tan 2.07} \right) = (102 + j0) \, \Omega. \end{aligned}$$

Thus, at the location  $A$  (at a distance  $d_{\max}$  from the load), the input impedance is purely real. If we add a shunt resistor  $R$  in parallel such that the combination is equal to  $Z_0$ , then the new  $Z_{\text{in}}$  at any point to the left of that location will be equal to  $Z_0$ .

Hence, we need to select  $R$  such that

$$\frac{1}{R} + \frac{1}{102} = \frac{1}{50}$$

or  $R = 98 \, \Omega$ .

---

**Problem 2.40** A 100-MHz FM broadcast station uses a 300- $\Omega$  transmission line between the transmitter and a tower-mounted half-wave dipole antenna. The antenna impedance is 73  $\Omega$ . You are asked to design a quarter-wave transformer to match the antenna to the line.

- (a) Determine the electrical length and characteristic impedance of the quarter-wave section.
- (b) If the quarter-wave section is a two-wire line with  $D = 2.5$  cm, and the wires are embedded in polystyrene with  $\epsilon_r = 2.6$ , determine the physical length of the quarter-wave section and the radius of the two wire conductors.

**Solution:**

(a) For a match condition, the input impedance of a load must match that of the transmission line attached to the generator. A line of electrical length  $\lambda/4$  can be used. From Eq. (2.97), the impedance of such a line should be

$$Z_0 = \sqrt{Z_{in}Z_L} = \sqrt{300 \times 73} = 148 \Omega.$$

(b)

$$\frac{\lambda}{4} = \frac{u_p}{4f} = \frac{c}{4\sqrt{\epsilon_r}f} = \frac{3 \times 10^8}{4\sqrt{2.6} \times 100 \times 10^6} = 0.465 \text{ m},$$

and, from Table 2-2,

$$Z_0 = \frac{120}{\sqrt{\epsilon}} \ln \left[ \left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} \right] \Omega.$$

Hence,

$$\ln \left[ \left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} \right] = \frac{148\sqrt{2.6}}{120} = 1.99,$$


which leads to

$$\left( \frac{D}{d} \right) + \sqrt{\left( \frac{D}{d} \right)^2 - 1} = 7.31,$$

and whose solution is  $D/d = 3.73$ . Hence,  $d = D/3.73 = 2.5 \text{ cm}/3.73 = 0.67 \text{ cm}$ .

---

**Problem 2.44** For the circuit shown in Fig. P2.44, calculate the average incident power, the average reflected power, and the average power transmitted into the infinite  $100\text{-}\Omega$  line. The  $\lambda/2$  line is lossless and the infinitely long line is slightly lossy. (Hint: The input impedance of an infinitely long line is equal to its characteristic impedance so long as  $\alpha \neq 0$ .)

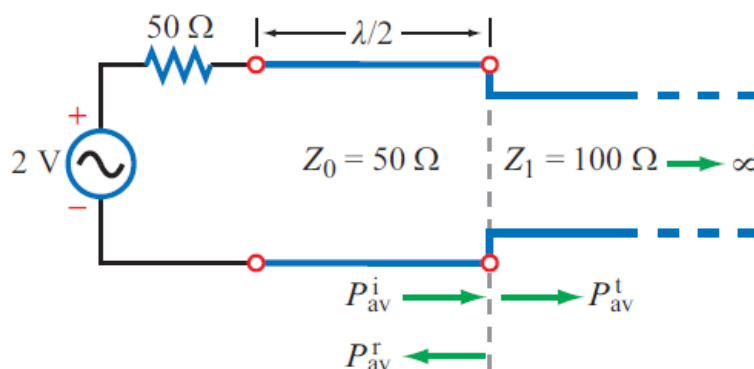

**Figure P2.44:** Circuit for Problem 2.44.

**Solution:** Considering the semi-infinite transmission line as equivalent to a load (since all power sent down the line is lost to the rest of the circuit),  $Z_L = Z_1 = 100\text{ }\Omega$ . Since the feed line is  $\lambda/2$  in length, Eq. (2.96) gives  $Z_{in} = Z_L = 100\text{ }\Omega$  and  $\beta l = (2\pi/\lambda)(\lambda/2) = \pi$ , so  $e^{\pm j\beta l} = -1$ . Hence

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3}.$$

Also, converting the generator to a phasor gives  $\tilde{V}_g = 2e^{j0^\circ}$  (V). Plugging all these results into Eq. (2.82),

$$\begin{aligned} V_0^+ &= \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right) = \left( \frac{2 \times 100}{50 + 100} \right) \left[ \frac{1}{(-1) + \frac{1}{3}(-1)} \right] \\ &= 1e^{j180^\circ} = -1 \text{ (V)}. \end{aligned}$$

From Eqs. (2.104), (2.105), and (2.106),


$$\begin{aligned} P_{av}^i &= \frac{|V_0^+|^2}{2Z_0} = \frac{|1e^{j180^\circ}|^2}{2 \times 50} = 10.0 \text{ mW}, \\ P_{av}^r &= -|\Gamma|^2 P_{av}^i = -\left| \frac{1}{3} \right|^2 \times 10 \text{ mW} = -1.1 \text{ mW}, \\ P_{av} &= P_{av}^t = P_{av}^i + P_{av}^r = 10.0 \text{ mW} - 1.1 \text{ mW} = 8.9 \text{ mW}. \end{aligned}$$

**Problem 2.47** Use the Smith chart to find the reflection coefficient corresponding to a load impedance of

- (a)  $Z_L = 3Z_0$
- (b)  $Z_L = (2 - j2)Z_0$
- (c)  $Z_L = -j2Z_0$
- (d)  $Z_L = 0$  (short circuit)

**Solution:** Refer to Fig. P2.47.

- (a) Point  $A$  is  $z_L = 3 + j0$ .  $\Gamma = 0.5e^{0^\circ}$
- (b) Point  $B$  is  $z_L = 2 - j2$ .  $\Gamma = 0.62e^{-29.7^\circ}$
- (c) Point  $C$  is  $z_L = 0 - j2$ .  $\Gamma = 1.0e^{-53.1^\circ}$
- (d) Point  $D$  is  $z_L = 0 + j0$ .  $\Gamma = 1.0e^{180.0^\circ}$

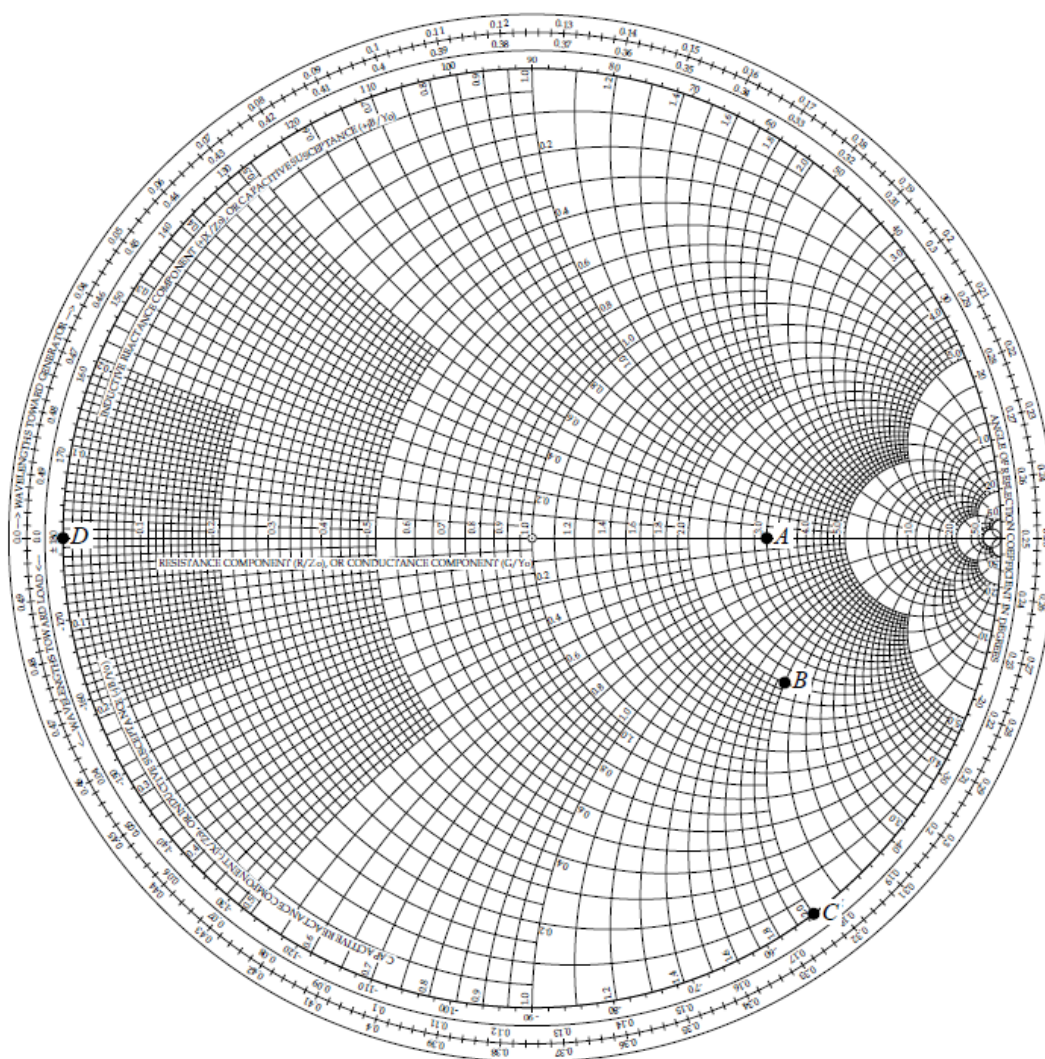


**Figure P2.47:** Solution of Problem 2.47.



**Problem 2.53** A lossless  $50\text{-}\Omega$  transmission line is terminated in a load with  $Z_L = (50 + j25)\text{ }\Omega$ . Use the Smith chart to find the following:

- The reflection coefficient  $\Gamma$ .
- The standing-wave ratio.
- The input impedance at  $0.35\lambda$  from the load.
- The input admittance at  $0.35\lambda$  from the load.
- The shortest line length for which the input impedance is purely resistive.
- The position of the first voltage maximum from the load.

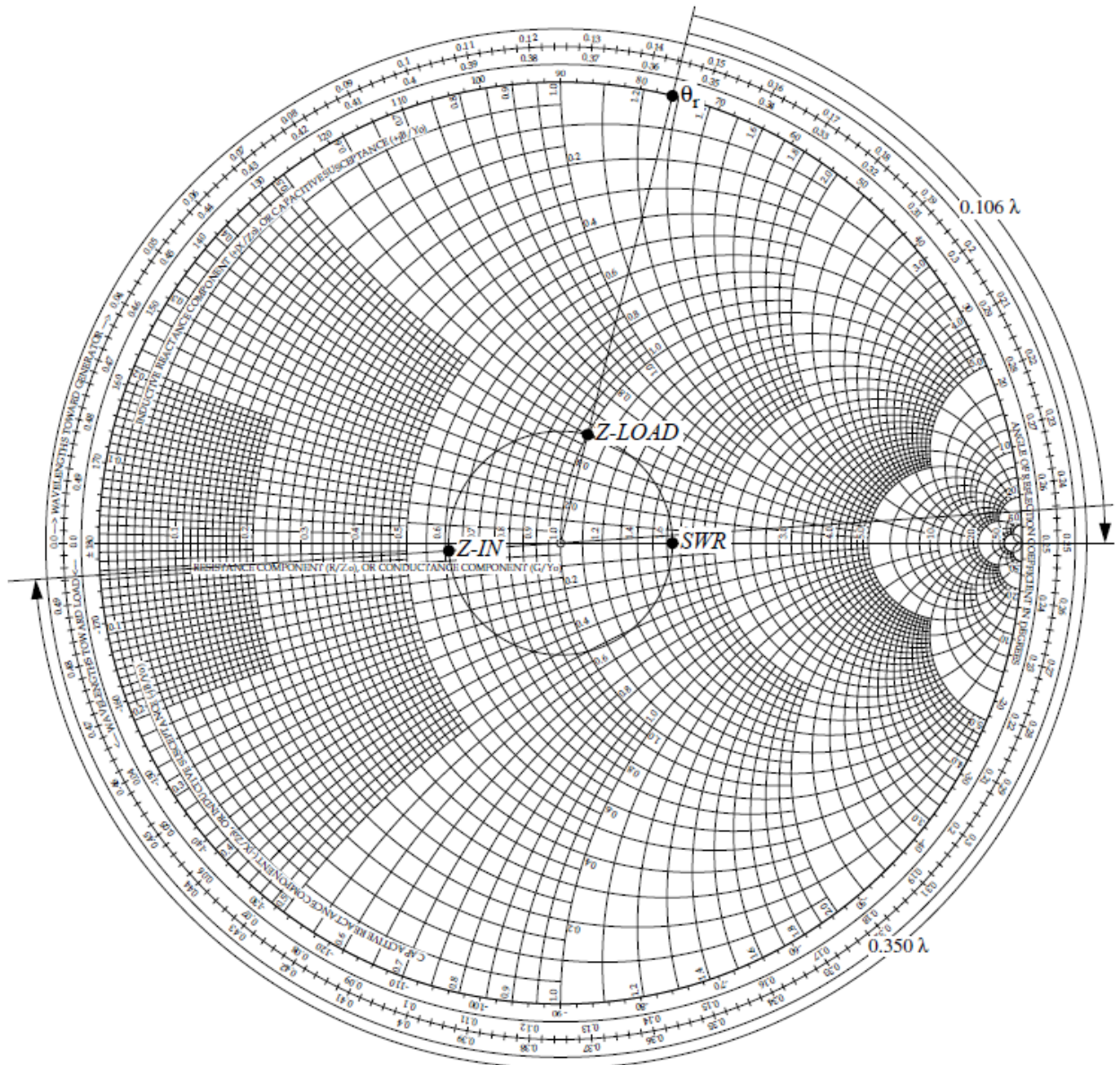

**Figure P2.53:** Solution of Problem 2.53.



**Solution:** Refer to Fig. P2.53. The normalized impedance

$$z_L = \frac{(50 + j25) \Omega}{50 \Omega} = 1 + j0.5$$

is at point *Z-LOAD*.

(a)  $\Gamma = 0.24e^{j76.0^\circ}$  The angle of the reflection coefficient is read of that scale at the point  $\theta_r$ .

(b) At the point *SWR*:  $S = 1.64$ .

(c)  $Z_{in}$  is  $0.350\lambda$  from the load, which is at  $0.144\lambda$  on the wavelengths to generator scale. So point *Z-IN* is at  $0.144\lambda + 0.350\lambda = 0.494\lambda$  on the WTG scale. At point *Z-IN*:

$$Z_{in} = z_{in}Z_0 = (0.61 - j0.022) \times 50 \Omega = (30.5 - j1.09) \Omega.$$

(d) At the point on the SWR circle opposite *Z-IN*,

$$Y_{in} = \frac{y_{in}}{Z_0} = \frac{(1.64 + j0.06)}{50 \Omega} = (32.7 + j1.17) \text{ mS}.$$

(e) Traveling from the point *Z-LOAD* in the direction of the generator (clockwise), the SWR circle crosses the  $x_L = 0$  line first at the point *SWR*. To travel from *Z-LOAD* to *SWR* one must travel  $0.250\lambda - 0.144\lambda = 0.106\lambda$ . (Readings are on the wavelengths to generator scale.) So the shortest line length would be  $0.106\lambda$ .

(f) The voltage max occurs at point *SWR*. From the previous part, this occurs at  $z = -0.106\lambda$ .

---